

BACHELOR OF TECHNOLOGY (C.B.C.S.) (2021-COURSE)

B. Tech. Sem - II E&TC :SUMMER- 2022

SUBJECT : DIGITAL ELECTRONICS

Day : Monday  
Date : 1/8/2022

S-24101-2022

Time : 10:00 AM-01:00 PM  
Max. Marks : 60

**N.B.**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Use of non-programmable calculator is **allowed**.
- 4) Assume suitable data **WHEREVER** necessary.
- 5) Draw neat diagram **WHEREVER** necessary.

**Q.1** Convert following numbers **(10)**  
 $(11001101.11)_2 = ( )_{10}$   
 $(45.2)_{10} = ( )_{10}$   
 $(453)_8 = ( )_{16}$   
 $(897)_{10} = ( )_8$   
 $(674)_{10} = ( )_{16}$

**OR**

**Q.1** Perform following using binary arithmetic **(10)**  
 $(01100 - 000111)$  using 2's compliment method  
 $(01000 - 01001)$  using 2's compliment method  
 $(23 - 48)$  using 1's compliment method  
 $(59 - 32)$  using 1's compliment method.

**Q.2** Solve and implement minimal expression for the following logic expression using **(10)**  
Quine Mc-Cluskey method  
 $Y = \sum_m (1, 5, 6, 12, 13, 14) + d(2, 4)$  .

**OR**

**Q.2** Prove De-morgan's Theorem and Duality Theorem. **(10)**

**Q.3** Explain in detail the design of look ahead carry generator. **(10)**

**OR**

**Q.3** Design 2 bit magnitude Comparator and draw realization using logic gates. **(10)**

**Q.4** Explain difference between combinational circuits and Sequential Circuits with **(10)**  
appropriate block diagram. Explain operation of SR Flipflop with circuit diagram  
and Truth Table.

**OR**

**Q.4** Draw block diagram and truth table of following flip flops. **(10)**  
i) MS JK flipflop  
ii) T flipflop  
iii) D flipflop.  
Explain any one application of flipflop

**Q.5** Design Asynchronous 3 bit binary UP / Down counter with mode control line. **(10)**

**OR**

**Q.5** Differentiate between following terms : **(10)**  
i) Moore and Mealy State Machine  
ii) Synchronous and Asynchronous sequential circuits.

**Q.6** Draw circuit diagram and explain working of 2 input TTL NAND Gate. **(10)**

**OR**

**Q.6** Implement the following function using PLA **(10)**  
 $F1 = \sum m (0 1 2 4)$   
 $F2 = \sum m (1 3 5 6)$   
Explain how to specify the size of PLA.

\*\*\*\*\*