

**BACHELOR OF TECHNOLOGY (C.B.C.S.) (2020 COURSE)**  
**B.Tech.Sem - IV ELECTRICAL :SUMMER- 2022**  
**SUBJECT : NETWORK & SYNTHESIS**

Day : Thursday  
 Date : 16-06-2022


**S-24549-2022**

Time : 10:00 AM-01:00 PM  
 Max. Marks : 60

**N.B.:**

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw neat and labeled diagram **WHEREVER** necessary.
- 4) Assume suitable data if necessary.

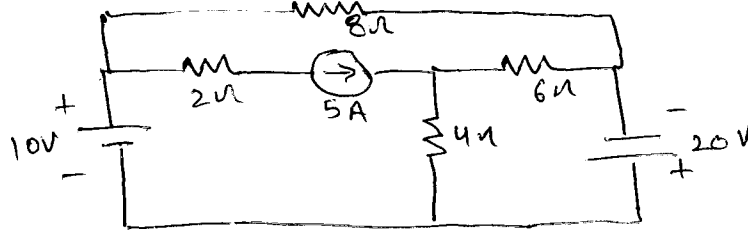**Q.1 a)** Find the current across  $4\Omega$  resistance using KVL. [05]




b) Explain the concept of duality and dual network. [05]

**OR**

**Q.1 a)** Explain the following terms: [05]


- i) Non-linear element    ii) Controlled voltage source    iii) Active element  
 iv) Bilateral element    v) Lumped element

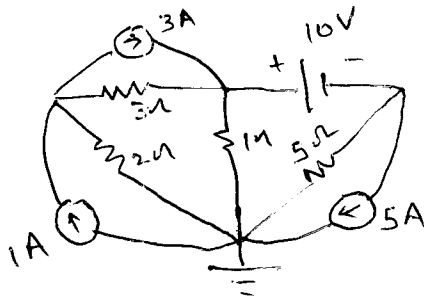b) Find the nodal voltages of given circuit. [05]



**Q.2 a)** Explain F-cut set and B-tie set matrix [05]

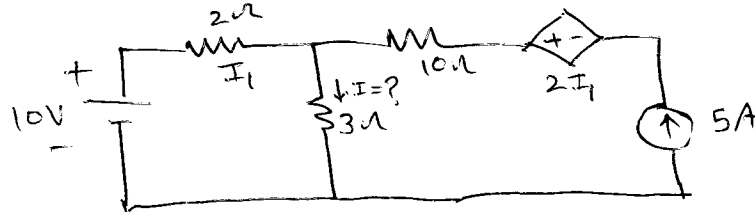
b) Calculate current across  $3\Omega$  resistance using superposition theorem. [05]



**OR**


**Q.2 a)** Explain reciprocal and Millman's theorem with example. [05]

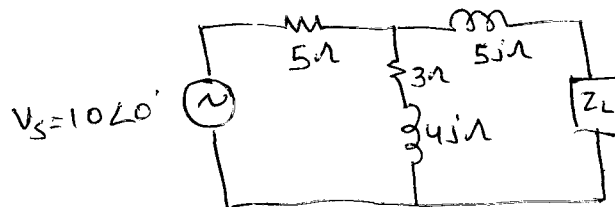b) Find the value of  $Z_L$  so that maximum power can be transferred. Also find maximum power value. [05]




**P.T.O.**

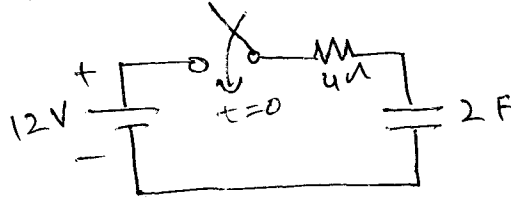Q.3 a) Find current,  $V_R$  and  $V_C$ . [05]




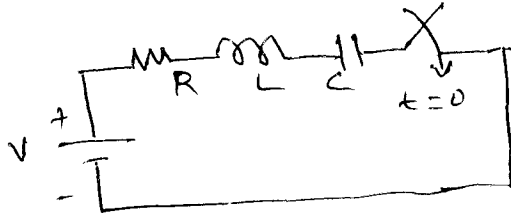b) Find  $V_R$ ,  $V_L$  and  $V_C$  values. [05]



OR

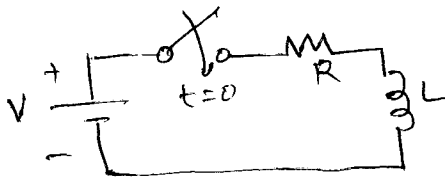
Q.3 a) Find  $V_R$  and  $V_L$  values. [05]



b) Explain RLC circuit with sinusoidal excitation. [05]

Q.4 a) Explain final value theorem. [05]

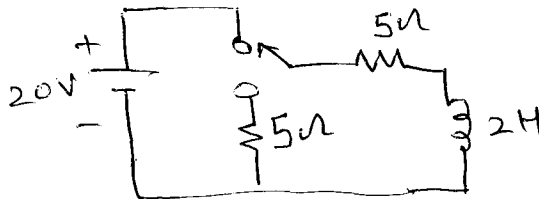
b) Switch is moved from 1 to 2 at time  $t = 0$ . The steady state current having previously established in RL circuit. Find  $i(t)$  after switching. [05]




OR

Q.4 a) Find the laplace transform of  $f(t) = e^{-at} \cos wt$ . [05]

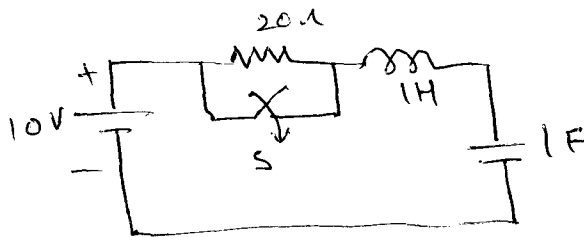b) Switch is closed at  $t = 0$ . Find voltage across resistor, inductor and capacitor. [05]



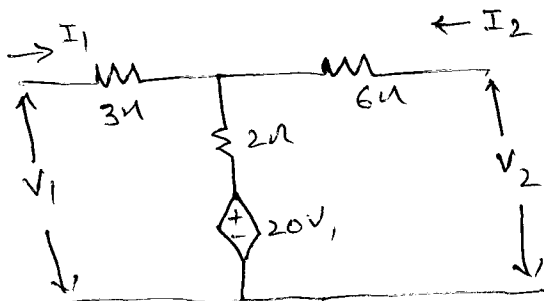
Q.5 a) Find z and h parameters of given circuit. [05]



b) Explain low pass and high pass filters with example. [05]

OR

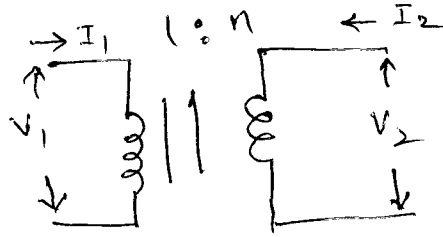Q.5 a) Find z, y, ABCD and h – parameters. [05]




b) Explain m-derived Low pass and High pass filters. [05]

Q.6 a) Explain the concept of poles, zeros, and transfer function and system stability relationship with pole zeros. [05]

b) Explain parallel resonance to find  $f_0$  and  $Q_0$ . [05]

OR

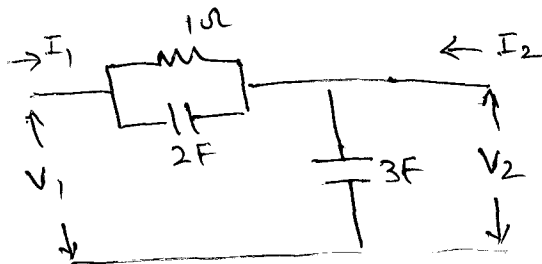Q.6 a) Find  $\frac{I_1}{V_2}$  for given circuit, also find pole zero and stability of ratio  $\frac{I_1}{V_2}$ . [05]



b) Explain why system is stable when pole zeros are on LHS of s-plane with example. [05]

\* \* \* \*