

BACHELOR OF TECHNOLOGY (C.B.C.S.) (2021-COURSE)
B. Tech. Sem - I E& C :SUMMER- 2022
SUBJECT : ELECTRICAL TECHNOLOGY

Day : Thursday
Date : 21-07-2022

S-24086-2022

Time : 10:00 AM-01:00 PM
Max. Marks : 60

N. B. :

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.

-
- Q.1** a) Explain star to delta conversion with neat diagram. (05)
b) Explain Kirchhoff's voltage and current law. (05)

OR

- a) Explain delta to star transformation with neat diagram. (05)
b) Explain maximum power transfer theorem with neat diagram. (05)

- Q.2** a) Explain effective value from factor and peak factor of sinusoidal waveform. (05)
b) What are different causes of low power factor? (05)

OR

- a) Analyze parallel R-L-C circuit. (05)
b) Explain resonance in series R-L-C circuit. (05)

- Q.3** a) How to determine efficiency and regulation of single phase transformer? (05)
b) Explain construction of 3-phase transformer. (05)

OR

- a) Draw diagram of auto-transformer and explain in brief. (05)
b) Explain Faraday's law of electromagnetic induction. (05)

- Q.4** a) Explain principle of electro mechanical energy conversion. (05)
b) Explain different applications of d.c. motor. (05)

OR

- a) Derive torque equation of d.c. motor. (05)
b) Explain principle of operation of single phase induction motor. (05)

- Q.5** a) Explain in brief about safe disposal of batteries. (05)
b) Explain construction of Nickel Cadmium battery. (05)

OR

- a) How to take care and maintenance of lead acid batteries. (05)
b) Explain general idea of solar panel and its applications. (05)

- Q.6** a) Explain interconnections between two-port parameters. (05)
b) What are ABCD parameters? Explain with equations. (05)

OR

- a) Explain condition for Reciprocity and symmetry in two port networks. (05)
b) What are Z & Y parameters in two port networks? (05)

* * * * *