

**BACHELOR OF TECHNOLOGY (C.B.C.S.) (2020 COURSE)**

**B.Tech.Sem - III E&C : : SUMMER - 2022**

**SUBJECT : SWITCHING THEORY & LOGIC DESIGN**

Day : Tuesday

Date : 31-05-2022

**S-24593-2022**

Time : 02:30 PM-05:30 PM

Max. Marks : 60

---

**N.B.**

- 1) All questions are **COMPULSORY**.
  - 2) Figures to the **RIGHT** indicate **FULL** marks.
  - 3) Use of non-programmable calculator is **ALLOWED**.
  - 4) Assume suitable data **WHEREVER** necessary.
- 

**Q.1** Convert the following numbers from Decimal to Octal and then to binary. (10)  
i) 375    ii) 249.

**OR**

**Q.1** For the logic expression :  $Y = A\bar{B} + \bar{A}B$  , (10)  
i) obtain the truth table  
ii) name the operation performed  
iii) realise this operation using AND, OR, NOT gates.

**Q.2** Prove the following using De Morgans theorems : (10)

- i)  $AB + CD = \overline{\overline{AB} \cdot \overline{CD}}$  .
- ii)  $(A+B) \cdot (C+D) = \overline{\overline{A+B} + \overline{C+D}}$  .

**OR**

**Q.2** Minimize the following function and realise using minimum number of gates (10)  
 $F = \sum m(0,3,5,6,9,10,12,15)$  .

**Q.3** Design and explain full subtractor circuit using two half subtractors and (10)  
realisation of full subtractor using NAND gates.

**OR**

**Q.3** Design a 32:1 multiplexer using two 16:1 multiplexer IC. (10)

**Q.4** Design 3 bit Binary counter. (10)

**OR**

**Q.4** Explain the operation of the bi-directional shift register. (10)

**Q.5** Differentiate between (10)

- i) RAM and ROM
- ii) Volatile memory and non-volatile memory.

**OR**

**Q.5** Explain any 5 characteristics of Digital IC. (10)

**Q.6** Explain in detail VLSI design flow (with reference to EDA tool). (10)

**OR**

**Q.6** Write short note on : (10)

- i) data flow
- ii) Structural modeling

\*\*\*\*\*