

.....
BACHELOR OF SCIENCE (CBCS-2018 COURSE)
T. Y. B. Sc. Sem-V : WINTER- 2022
SUBJECT : PHYSICS : ADVANCED ELECTRONICS

Day : Wednesday

Time : 02:00 PM-05:00 PM

Date : 14-12-2022

W-18409-2022

Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
 - 2) Figures to the **RIGHT** indicate **FULL** marks.
-

Q 1. Attempt any **Two** of the following. **(12)**

- (a) Explain class A push pull amplifier with circuit diagram.
- (b) Describe P-channel depletion type JFET with diagram. Draw its characteristic curve & explain.
- (c) Explain the astable multivibrator by using IC 555 with Block diagram and circuit diagram

Q 2. Attempt any **Two** of the following. **(12)**

- (a) Explain high voltage regulator by using IC 723 with circuit diag. Obtain necessary formulae.
- (b) Obtain an expression for efficiency of transformer coupled amplifier.
- (c) Design the circuit of square wave generator by using IC 555. Given $f = 2 \text{ KHz}$ duty cycle = 0.6 and $C = 0.1 \mu\text{F}$

Q 3. Attempt any **Two** of the following. **(12)**

- (a) Explain the application of operational amplifier as adder with diagram.
- (b) Describe class A, Class B, class C and class AB amplifier with diagram.
- (c) Explain Wein Bridge Oscillator with circuit diagram. Derive the necessary formula.

Q 4. Attempt any **Three** of the following. **(12)**

- (a) Explain differential amplifier with circuit diagram. Draw its symbol.
- (b) Describe the Hartley oscillator with circuit diagram.
- (c) Design the power supply of 6 V, 40 mA by using IC 723.
- (d) Explain the application of operational amplifier as integrator with diagram.

Q 5. Attempt any **Four** of the following. **(12)**

- (a) Explain AC amplifier by using N-channel depletion type MOSFET with circuit diagram.
- (b) Write a short note on DC load line.
- (c) Write a short note on crossover distortion in case of class B push pull amplifier.
- (d) Explain non-inverting amplifier by using operational amplifier.
- (e) What are the types of feedbacks? Obtain the expression for Barkhausen Criteria.
- (f) Explain the principle of regulated power supply with diagram.

* * * *