

.....
BACHELOR OF SCIENCE (COMPUTER SCIENCE) (CBCS - 2018 COURSE)
F.Y.B.Sc.(Computer Science) Sem-I : WINTER- 2022
SUBJECT : PRINCIPLES OF DIGITAL ELECTRONICS-I

Day : Friday

Time : 10:00 AM-01:00 PM

Date : 16-12-2022

W-20071-2022

Max. Marks : 60

N.B.

- 1) All questions are **COMPULSORY**.
- 2) Figures to the right indicate **FULL** marks.
- 3) Draw diagrams **WHEREVER** necessary.

- Q.1** Answer **ANY TWO** of the following: (12)
- a) Explain the working of 4:1 multiplexer with necessary diagram and truth table.
 - b) Construct the Hamming code for the data 1010 with odd parity.
 - c) Give the symbol, Boolean equations and truth table for the following gates:
i) NAND ii) EX-OR iii) AND
- Q.2** Answer **ANY TWO** of the following: (12)
- a) Explain the working of decimal to BCD encoder with logic diagram.
 - b) Reduce the following four variable functions to its minimum sum-of-product-form:
$$Y = \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}$$
Also implement it by using logic gates.
 - c) With neat diagram explain 4-bit parallel adder circuit.
- Q.3** Answer **ANY TWO** of the following: (12)
- a) Explain the working of 1:4 demultiplexer with necessary diagram and truth table.
 - b) Explain the working of octal-to-binary priority encoder.
 - c) With logic diagram and truth table explain the working of 1-of-4 decoder.
- Q.4** Answer **ANY THREE** of the following: (12)
- a) Draw the logic diagram and give the truth table for:
i) Half adder ii) Half subtractor
 - b) Construct NOT and OR gate using NOR gate.
 - c) Simplify the following expressions:
i) $\overline{AB} + \overline{A} + AB$
ii) $\left[\overline{AB}(C + BD) + \overline{AB} \right] C$
 - d) Define the following parameters for logic families:
i) Speed of operation ii) Power dissipation
iii) Noise immunity iv) Fan-out
- Q.5** Answer **ANY FOUR** of the following: (12)
- a) Construct OR and AND gates using NAND gates.
 - b) State and prove De-Morgan's first theorem.
 - c) Perform the following conversions:
i) $(132)_{10} = (?)_8$ ii) $(1010111001011)_2 = (15CB)_{16}$
iii) $(145)_{10} = (?)_2$
 - d) Explain the concept tree multiplexing.
 - e) Perform the following subtraction using 2's complement method
 $(011001)_2 - (10110)_2$
 - f) Explain the concept of analog multiplexer.
- * * * *