

BACHELOR OF SCIENCE (COMPUTER SCIENCE) (CBCS - 2018 COURSE)
F.Y.B.Sc.(Computer Science) Sem-I : WINTER- 2022
SUBJECT : PRINCIPLES OF ANALOG ELECTRONICS-I

Day : Wednesday

Time : 10:00 AM-01:00 PM

Date : 14-12-2022

W-20070-2022


Max. Marks : 60

N.B.:

- 1) All questions are **COMPULSORY**.
- 2) Figures to the **RIGHT** indicate **FULL** marks.
- 3) Draw neat labeled diagram **WHEREVER** necessary.
- 4) Use of **CALCULATOR** is allowed.

Q.1 Answer **ANY TWO** of the following: [12]

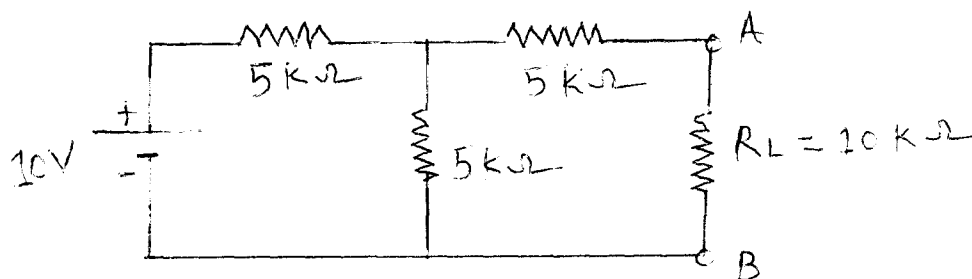- a) With necessary diagram explain the construction and working of n-channel JFET.
- b) i) Give the statement for Thevenin's Theorem.
ii) Find the current through load using Thevenin's theorem.



- c) Explain the working principle of UJT with necessary diagram.

Q.2 Answer **ANY TWO** of the following: [12]

- a) Explain the working of npn transistor with neat diagram.
- b) Derive the equation for growth and decay of current in R-C circuit.
- c) Explain the construction of n-channel MOSFET with necessary diagram. Also draw symbol for it.

Q.3 Answer **ANY TWO** of the following: [12]

- a) With necessary diagram explain the output characteristic curve for transistor in CE-mode.
- b) Explain the colour code theory for fixed resistors. Also explain one example of it.
- c) Draw well labelled diagram for single stage R-C coupled amplifier. Explain it.

Q.4 Answer **ANY THREE** of the following: [12]

- a) Define capacitance. Explain the action of electrolytic capacitor with necessary diagram.
- b) Give the statement for: Norton's theorem and maximum power transfer theorem.
- c) Find the value of α , I_B and I_E of a transistor if $I_C = 10$ mA and $\beta = 200$.
- d) With necessary diagram explain class A and B amplifiers.

Q.5 Answer **ANY FOUR** of the following: [12]

- a) State three points of difference between BJT and FET.
- b) Explain the following terms of JFET:
i) Drain resistance ii) Transconductance iii) Amplification factor
- c) Draw symbols for:
i) PNP transistor ii) SCR iii) Step-down transformer
- d) Define α and β . Derive the expression for α in terms of β .
- e) State and explain types of thermistors.
- f) Give the classification of amplifiers on the basis of frequency.